


LOGIC CIRCUITS

Explain the working of half adder with logic diagram & truth table

* Half adder is a combinational logic circuit that performs addition of 2 bits.

* It accepts 2 inputs (augend & addend) & produces 2 outputs a sum & a carry bit

LOGIC SYMBOL

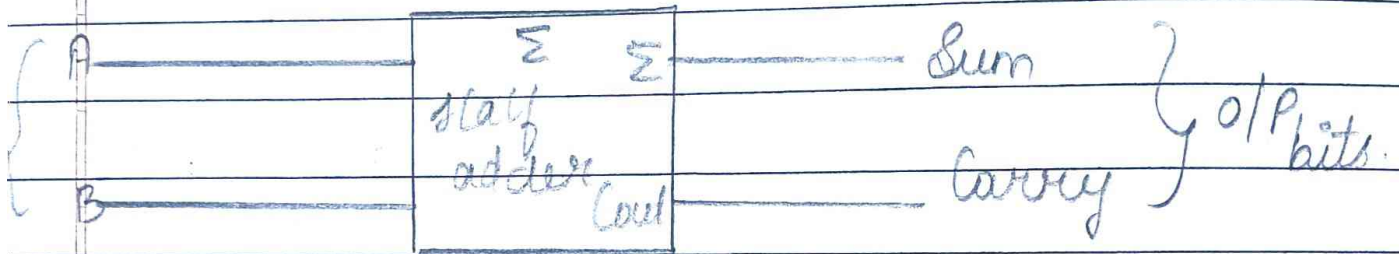

Truth Table.

Inputs		Outputs	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


* Carry bit is 1 only when both A & B are 1

$$\therefore \text{Cout} = A \cdot B$$

* Sum bit is 1 when both inputs are unequal


$$\therefore \text{Sum } (\Sigma) = A \oplus B$$

Logic diagram.

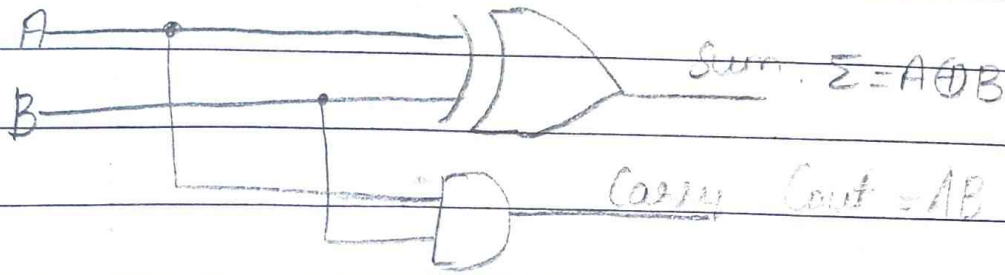

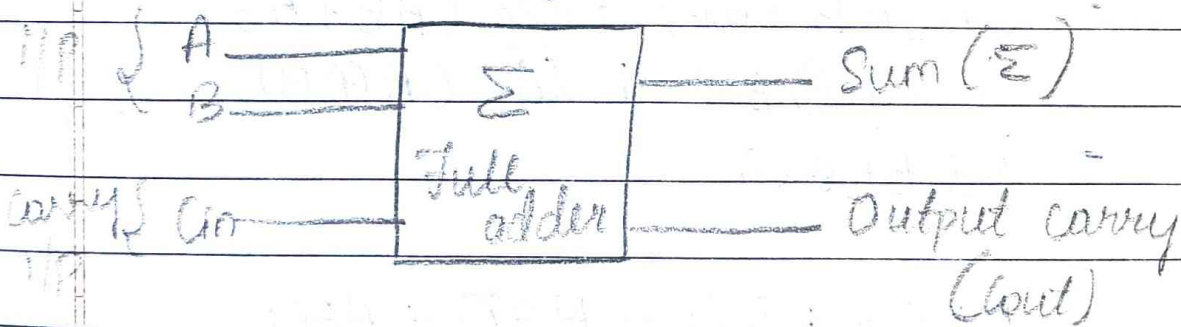2. Explain the working of full adder with logic diagram & truth table.

A full adder is C.L.C that accepts 2 binary i/p's & an carry input. It generates a sum o/p & an carry o/p.
 Logic Symbol.



Truth table.

Inputs			Outputs	
A	B	Cin	Sum (Σ)	Cout
0	0	0	0	0
0	0	1	1	0

0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

* From half adder the ^{output} ~~input~~ of sum is A, B is XORed. Now the ^{input} ~~input~~ carry bit C_{in} is to be added, so C_{in} is XORed with $A \oplus B$.


$$\therefore \text{Sum} = (A \oplus B) \oplus C_{in}$$

Boolean expressions are:-

$$\begin{aligned} \text{Sum} &= \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in} \\ &= C_{in}(\bar{A}\bar{B} + AB) + \bar{C}_{in}(\bar{A}B + A\bar{B}) \\ &= C_{in}(A \oplus B) + \bar{C}_{in}(A \oplus B) \\ &= (A \oplus B) \oplus C_{in} \end{aligned}$$


$$\begin{aligned} \text{Carry} &= \bar{A}BC_{in} + A\bar{B}C_{in} + AB\bar{C}_{in} + ABC_{in} \\ &= C_{in}(\bar{A}B + AB) + AB(\bar{C}_{in} + C_{in}) \\ &= C_{in}(A \oplus B) + AB(1) \\ &= C_{in}(A \oplus B) + AB \end{aligned}$$

Logic circuit.

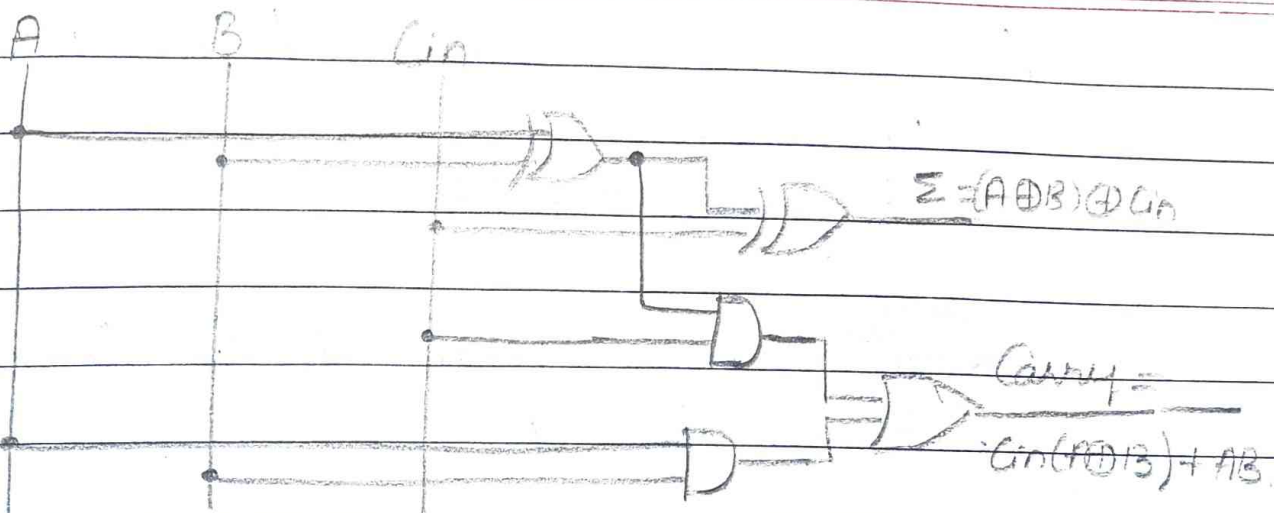

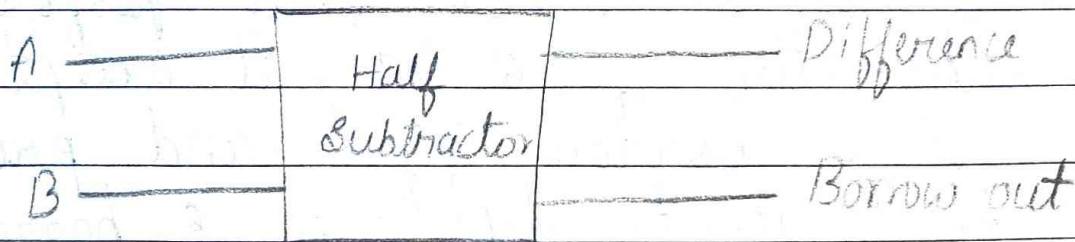3. Explain the working of half subtractor with logic diagram & truth table.

It is a C.L.C that subtracts performs subtraction of 2 binary bits. It accepts 2 i/p's (Minuend & subtrahend) & gives 2 o/p's a difference & a borrow bit.



Truth Table


Inputs		Outputs	
A	B	Diff	Bout
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

* Difference is 1 when both i/p's are unequal.

$$\therefore \text{Difference} = A \oplus B$$

* ^{Borrow out} ~~Sum~~ is high when A is 0 & B is 1

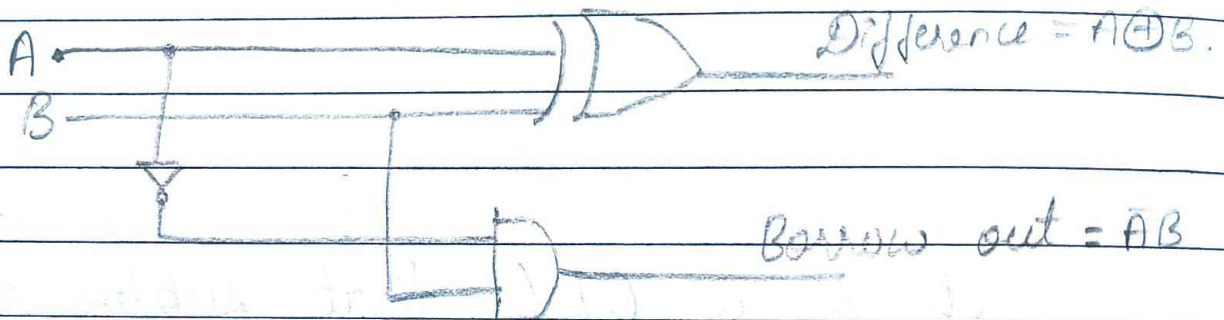
$$\therefore \text{Borrow out} = \bar{A}B$$



H.

Explain the working of a full subtractor with logic diagram & truth table.

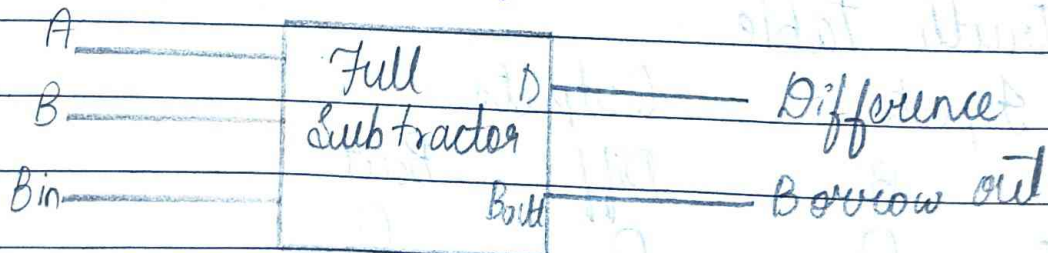It is a C.L.C that performs the subtraction of 2 bits. It accepts 2 i/p's and a borrow input and produces the outputs difference & borrow output.



Truth Table.

Inputs			Outputs	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


* From half subtractor the output of Difference $A \oplus B$ is X-ored. Now the input Bin is to be added. So Bin is X-ORed with $A \oplus B$.

$$\therefore \text{Difference} = (A \oplus B) \oplus Bin.$$

$$\begin{aligned} \text{Difference} &= \bar{A}\bar{B}Bin + \bar{A}B\bar{B}in + \bar{A}B\bar{B}in + AB\bar{B}in \\ &= Bin(\bar{A}\bar{B} + AB) + \bar{B}in(\bar{A}B + AB) \\ &= Bin(A \oplus B) + \bar{B}in(A \oplus B) \\ &= (A \oplus B) \oplus Bin. \end{aligned}$$

$$\begin{aligned} \text{Borrow out} &= \bar{A}\bar{B}Bin + \bar{A}B\bar{B}in + \bar{A}B\bar{B}in + AB\bar{B}in \\ &= Bin(\bar{A}\bar{B} + AB) + \bar{A}B(\bar{B}in + Bin) \\ &= Bin(\overline{A \oplus B}) + \bar{A}B(1) \end{aligned}$$
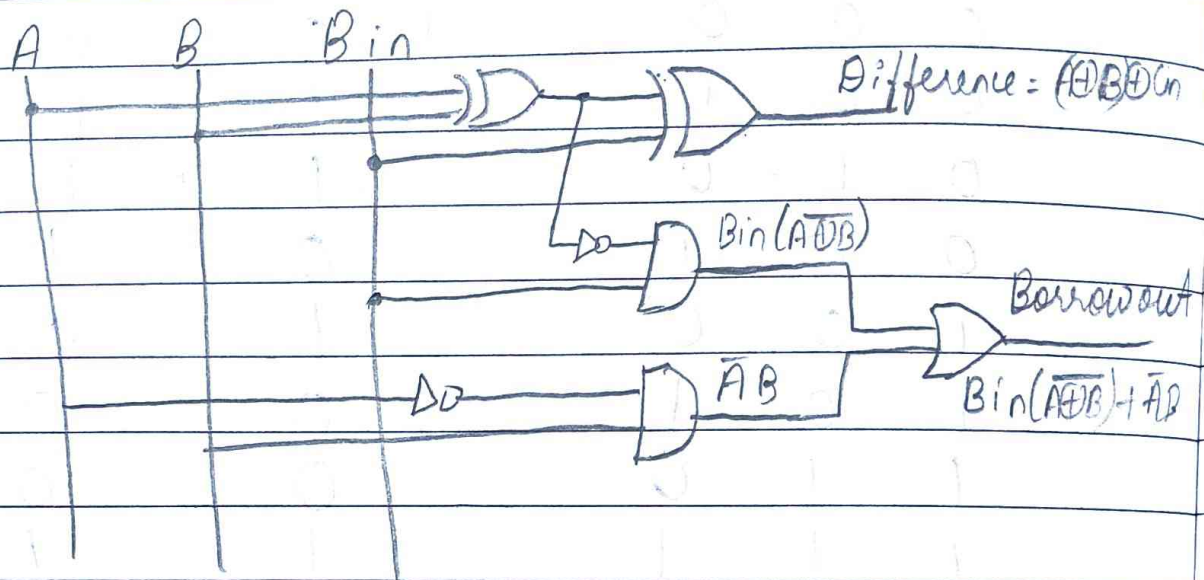
$$= \text{Bin}(\overline{A \oplus B}) + \overline{AB}$$





5. Write difference b/w half adder & full adder.

Half adder	Full adder
<ul style="list-style-type: none"> It adds 2 binary digits & generates sum & carry Carry obtained from previous addition can not be added. It consists of only one X-OR gate & 1 AND-gate. Used in calculators. 	<ul style="list-style-type: none"> It adds 3 binary digits & generates sum & carry Adds previous carry along with current inputs It consists of 2 X-OR gates, 2 AND gate & 1 OR gate Used in multiple

computers etc

bit addition, digital processors etc

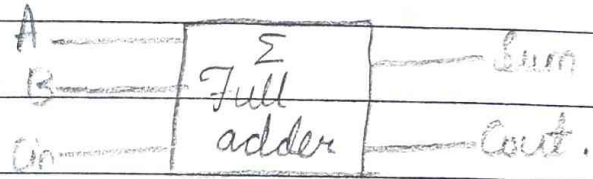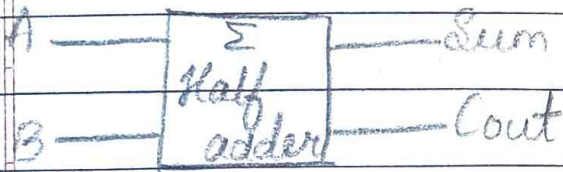

6. Define Encoder & Decoder.

Encoder.

It is a C.L.C that accepts a decimal or octal digit on its i/p's & converts it to a coded output such as BCD or Binary. It has 2^n i/p's & n o/p's

Eg:- Decimal to BCD encoder.

Decoder.

It is a C.L.C that converts coded info into a recognizable format. It has n inputs & 2^n o/p's.

Eg:- BCD to decimal decoder.

7. Explain with a neat ^{circuit} diagram & truth table & working of BCD to decimal decoder.

BCD to decimal decoder is also called

Boolean equations

$$D_0 = \bar{A}_3 \bar{A}_2 \bar{A}_1 \bar{A}_0$$

$$D_1 = \bar{A}_3 \bar{A}_2 \bar{A}_1 A_0$$

$$D_2 = \bar{A}_3 \bar{A}_2 A_1 \bar{A}_0$$

$$D_3 = \bar{A}_3 \bar{A}_2 A_1 A_0$$

$$D_4 = \bar{A}_3 A_2 \bar{A}_1 \bar{A}_0$$


$$D_5 = \bar{A}_3 A_2 \bar{A}_1 A_0$$

$$D_6 = \bar{A}_3 A_2 A_1 \bar{A}_0$$

$$D_7 = \bar{A}_3 A_2 A_1 A_0$$


$$D_8 = A_3 \bar{A}_2 \bar{A}_1 \bar{A}_0$$

$$D_9 = A_3 \bar{A}_2 \bar{A}_1 A_0$$

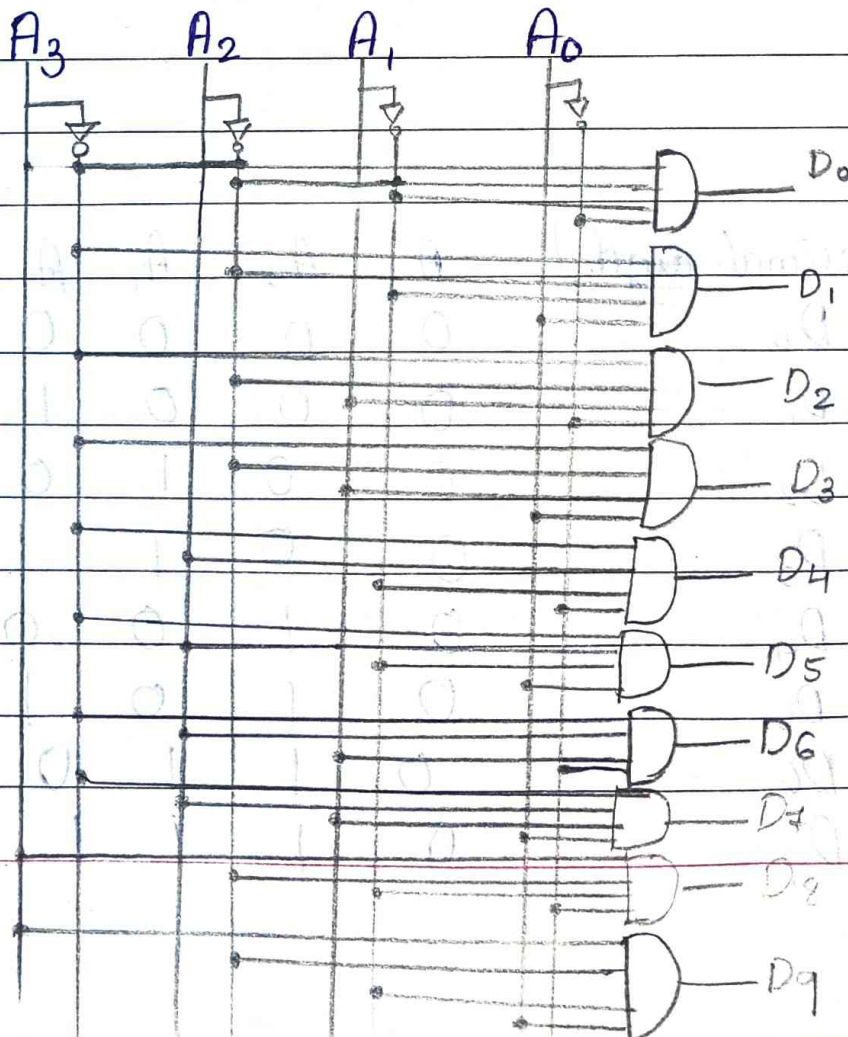

8. Explain with a neat circuit & truth table the working of Decimal to BCD encoder.

It is called as 10-4 line encoder.

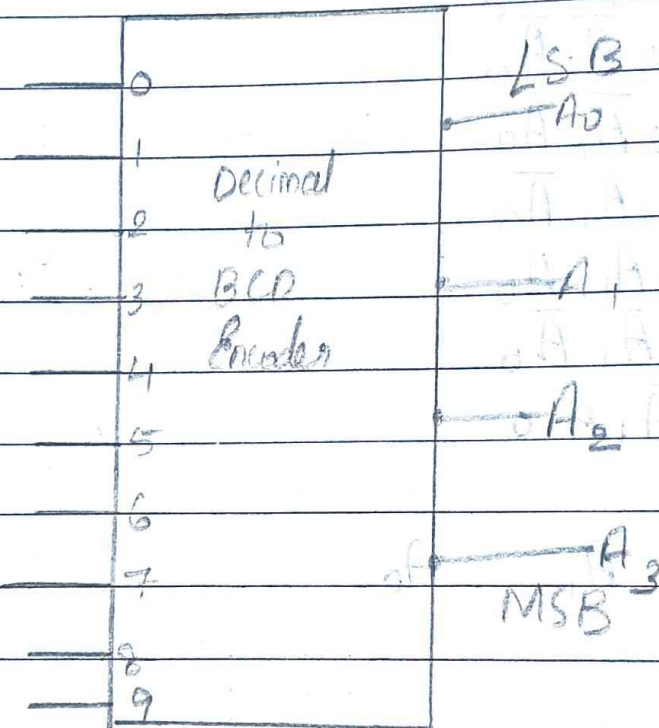

Input (Decimal digit)		A_3	A_2	A_1	A_0 (BCD code)
0	D_0	0	0	0	0
1	D_1	0	0	0	1
2	D_2	0	0	1	0
3	D_3	0	0	1	1
4	D_4	0	1	0	0
5	D_5	0	1	0	1
6	D_6	0	1	1	0
7	D_7	0	1	1	1


8	D_8	1	0	0	0
9	D_9	1	0	0	1

$$A_3 = D_8 + D_9$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$


$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_0 = D_1 + D_3 + D_5 + D_7 + D_9$$

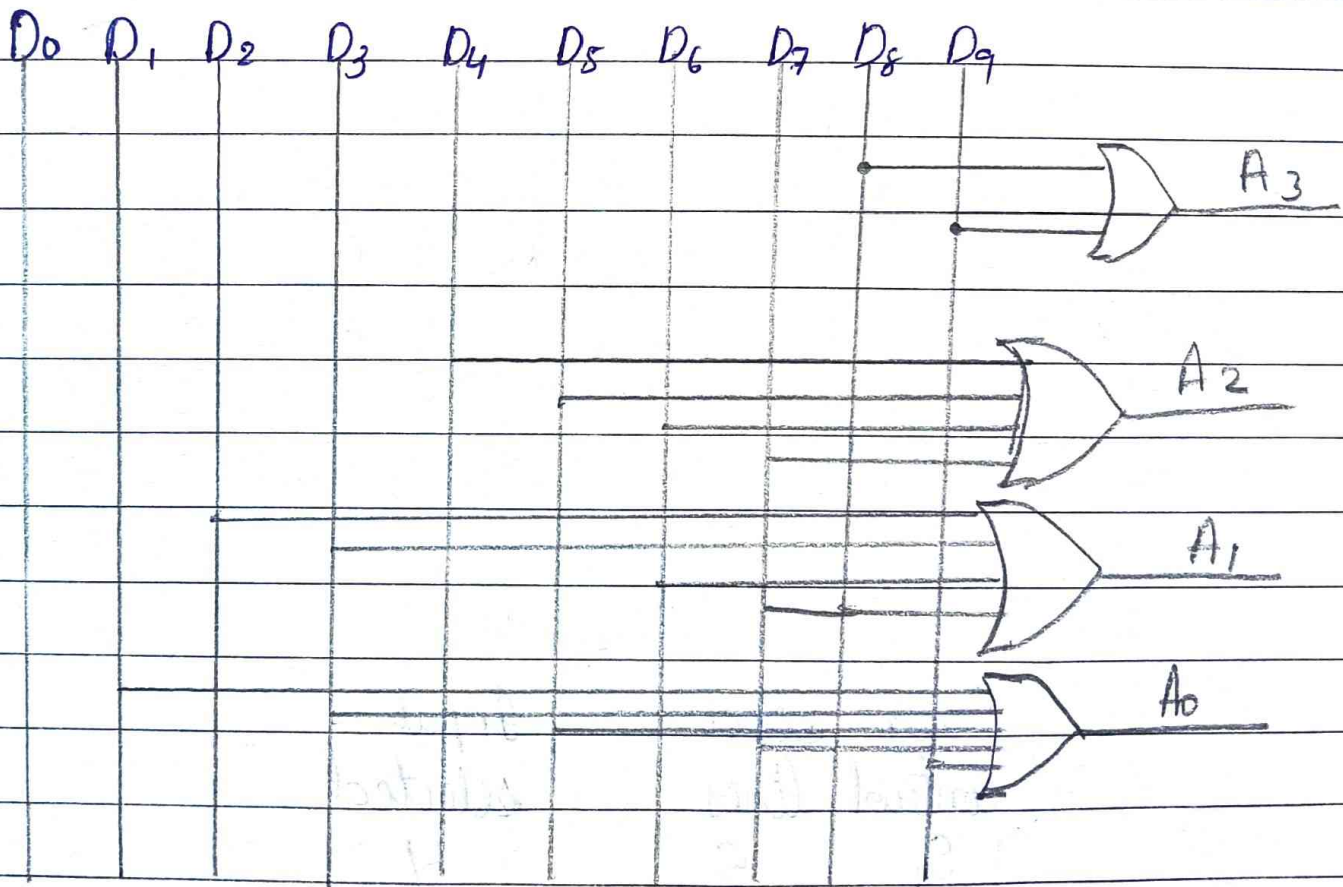

9. Explain with a neat circuit and truth table, the working of 4:1 Mux
- * Multiplexers also known as Data Selector
 - * It consists of many i/p's & single o/p
- A 4:1 MUX have 4 data i/p's & 1 o/p line with 2 data-select control lines.

Logic Symbol.

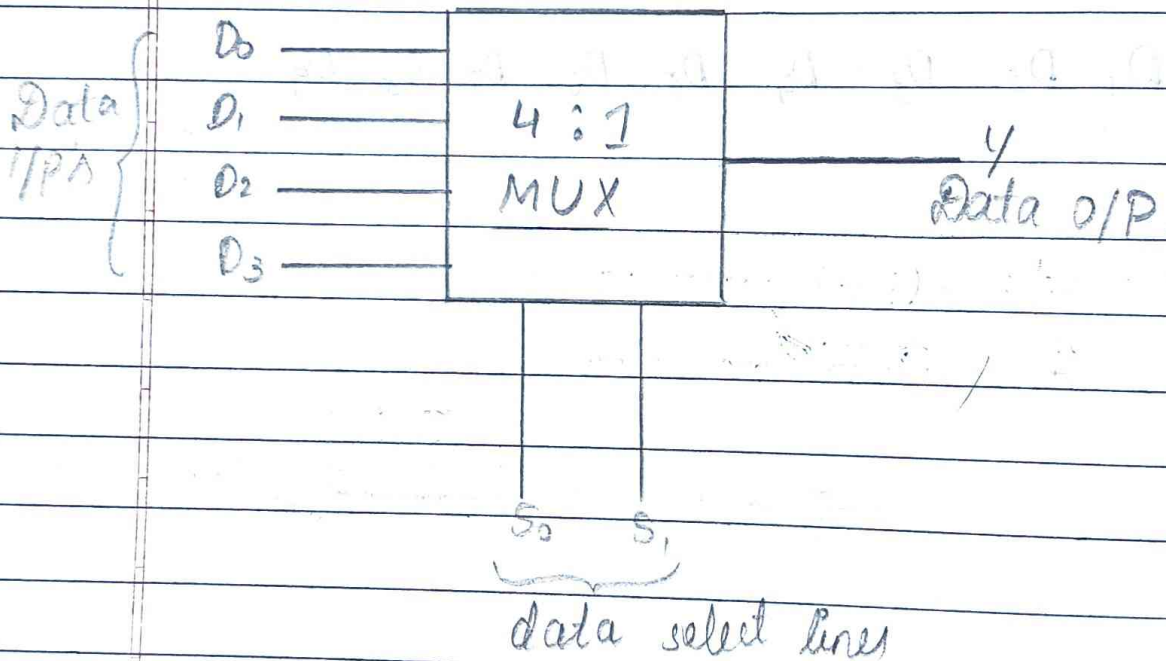

Data select control lines		Input selected
S_1	S_0	
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

Boolean expression,

$$Y = D_0 \bar{S}_1 \bar{S}_0 + D_1 \bar{S}_1 S_0 + D_2 S_1 \bar{S}_0 + D_3 S_1 S_0$$

i.e


output $Y = D_0$ if only $S_1 = 0$ $S_0 = 0$

output $Y = D_1$ if only $S_1 = 0$ $S_0 = 1$

output $Y = D_2$ if only $S_1 = 1$ $S_0 = 0$


Output $Y = D_3$ if only $S_1 = 1$ $S_0 = 1$

Logic diagram

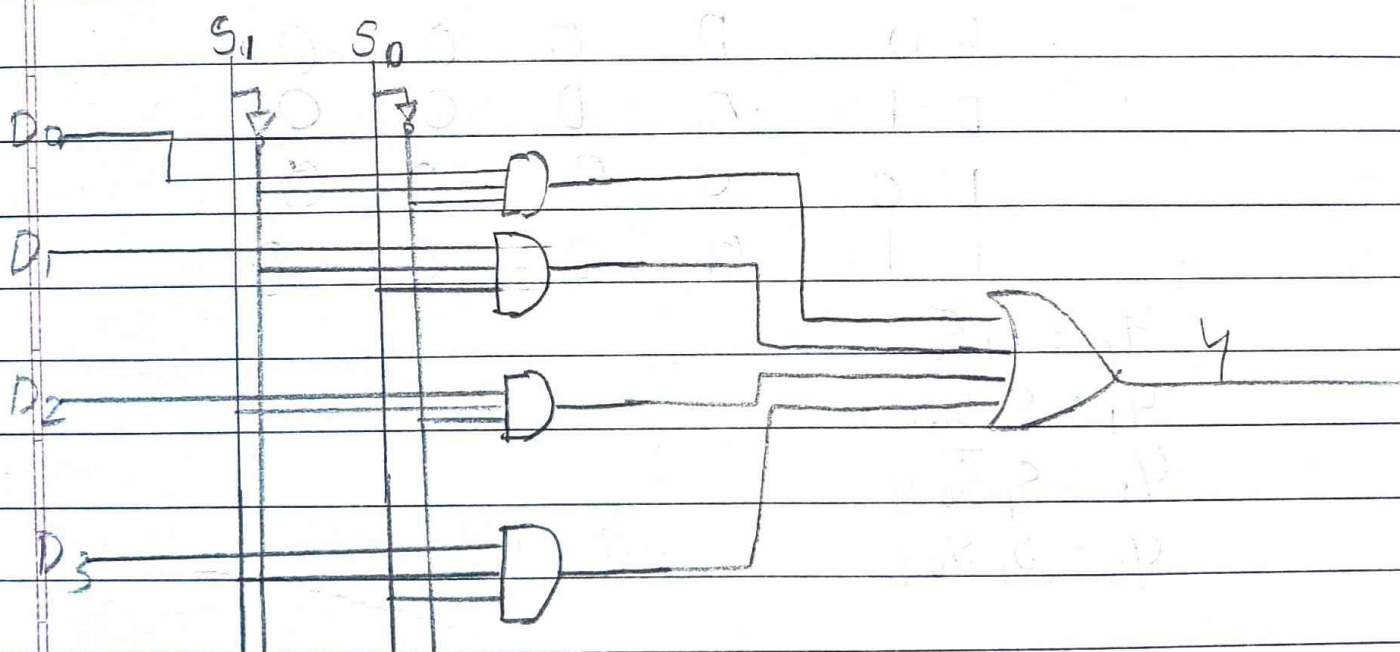

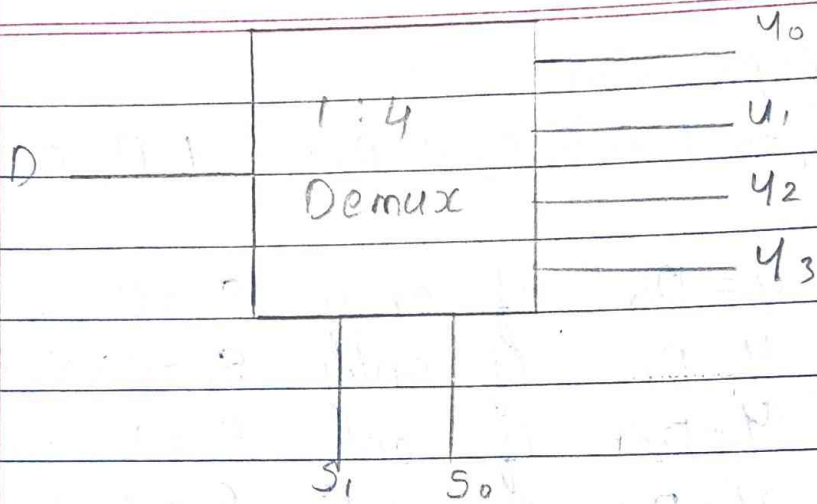10. Explain ^{with} a neat circuit & truth table, working of demux.

They are also known as Data Distributors. It consists of m i/p & many o/p's. A 1:4 demux have 1 i/p 2 select line & 4 outputs.



Truth Table


I/P's		O/P			
S_1	S_0	Y_0	Y_1	Y_2	Y_3
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

$$Y_0 = \bar{S}_1 \bar{S}_0 D$$


$$Y_1 = \bar{S}_1 S_0 D$$

$$Y_2 = S_1 \bar{S}_0 D$$


$$Y_3 = S_1 S_0 D$$

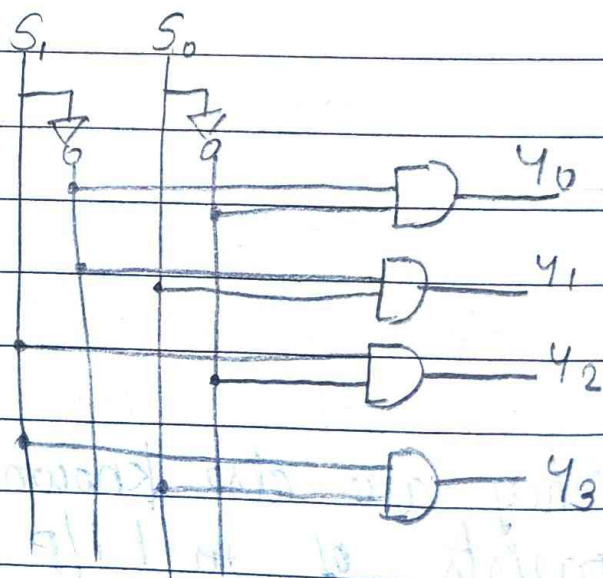

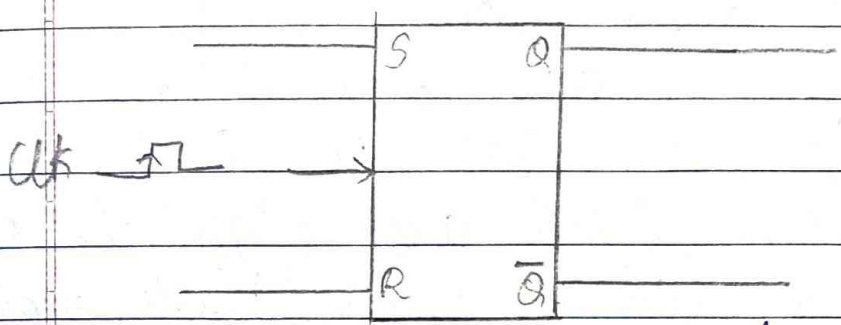11. Explain ^{SR} Flip-Flop with logic circuit diagram & truth Table.



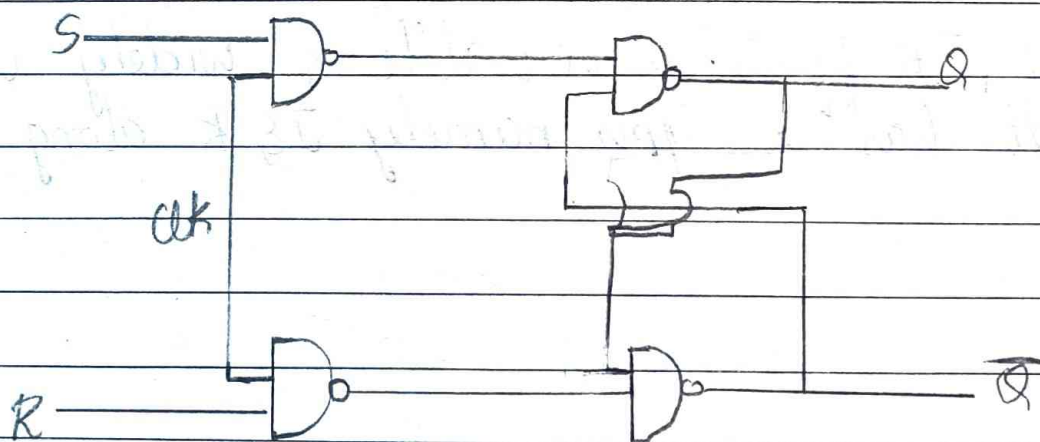Logic symbol for edge triggered flip-flop.



Inputs			Outputs		Comments
S	R	clk	Q	\bar{Q}	
0	0	1	Q	\bar{Q}	No change
0	1	1	0	1	Reset
1	0	1	1	0	Set
1	1	1	Q	\bar{Q}	Invalid.